 




Number:

Q1) Write the Verilog code for following combinational logic.


$$F(A, B, C, D) = \Sigma (0, 2, 6, 7, 8, 10, 15)$$

- 3) Complete the truth table for all possible inputs and corresponding outputs.
- 4) Please, write Verilog code without simplification.

Q3) Create a 4-bit prime number detector. The circuit has four inputs-N3, N2, N1, and N0—that correspond to a 4-bit number (N3 is the most significant bit) and one output P that is 1 when the input is a prime number and that is 0 otherwise.