



**WORCESTER POLYTECHNIC INSTITUTE
ELECTRICAL AND COMPUTER ENGINEERING
ECE2029 INTRODUCTION TO DIGITAL CIRCUIT DESIGN
FALL-B-2024**

Preliminary work for Experiment 1

This exemplary experiment is optional and it is to be conducted at home by yourself. Do not submit anything on this experiment.

- 1) Write a Verilog code to implement an alarm system using basic logic functions. This alarm system has 3 inputs;
- Door Open Sensor (**C**)
 - Motion Sensor (**B**)
 - Arm(Enable) Alarm (**A**)
- And one output;
- Alarm (**Z**)

Boolean expression of alarm system is: $Z = (B + C) * A$

Draw the logic circuit by hand, show the truth table and implement in Verilog. Test your design by creating a test bench.